 


# Lecture 04

## Modeling, Analysis and Simulation in Logic Design

逻辑设计中的建模、分析与仿真




Dr. Yinong Chen

IoT & Robotics Education  
Laboratory

# Engineering Design Process

## 工程设计过程

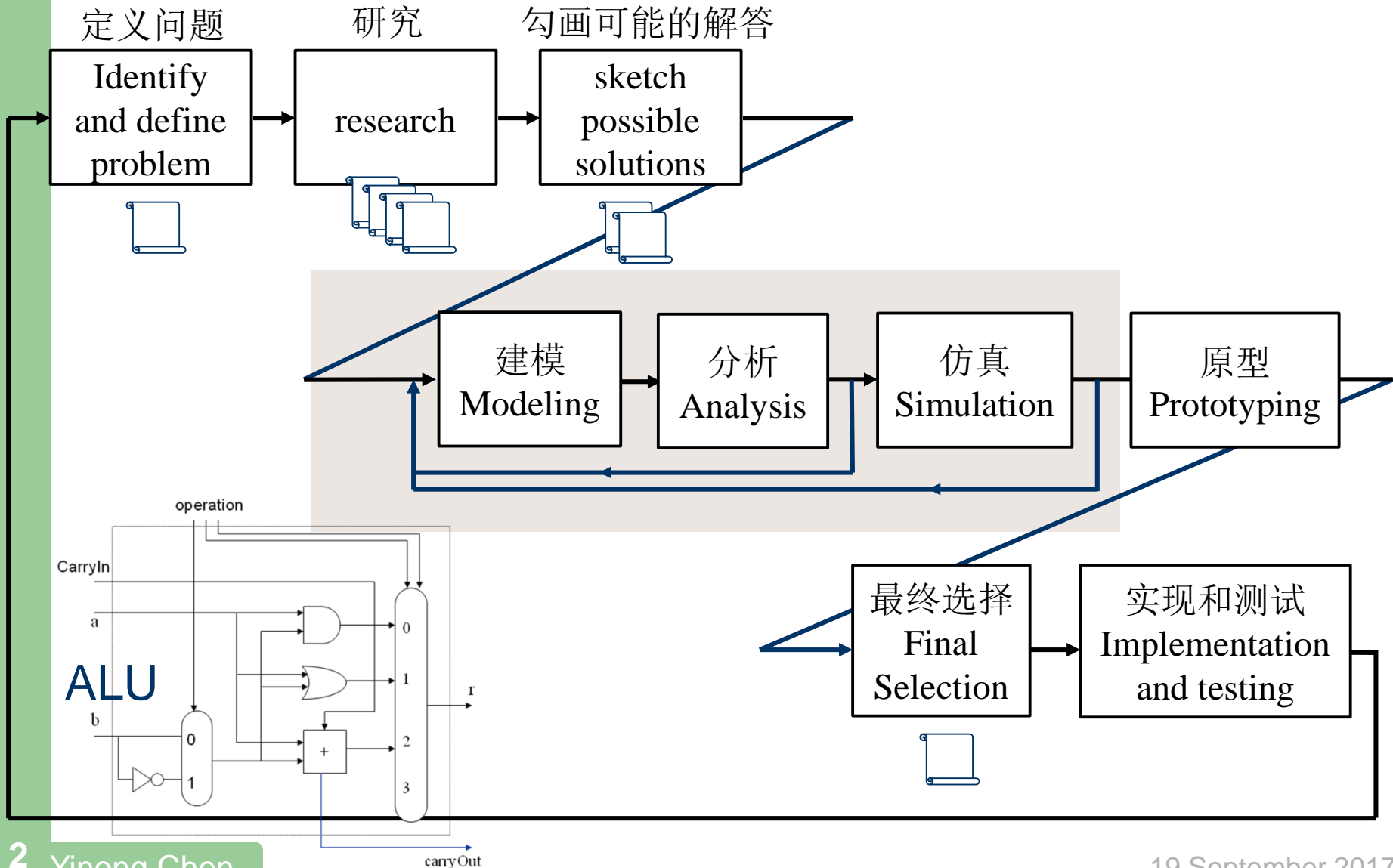

# Contents 内容

1

Logic Design and Modeling in Truth Table  
逻辑设计与用真值表的建模

2

Building Blocks of Digital Systems  
数字系统的构建块

3

Memory Design  
存储器设计

4

Arithmetic / Logic Unit (ALU) Design & Testing  
算术/逻辑部件ALU的设计与测试


5

Simulate ALU Design in VIPLE  
用VIPLE仿真ALU设计


# Logic Design: Analogue versus Digital

## 逻辑设计：模拟与数字


tank

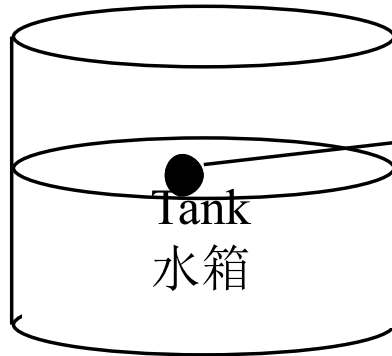


dial

 

infinite range of values

 

light : on / off  
finite set of values

 

# Propositional Logic and its Elements

## 命题逻辑及其构成要素

- Propositional logic is a language for modeling and specification 命题逻辑是一种建模和规范语言。
- Proposition: A statement that can either be true or false:  
命题：一个语句，它的值可以是真，或是假
  - One plus two is three
  - There are two Nobel prize winners at Arizona State University
  - The sky is blue
  - How old are you?
  - You must ride a bike to school!
- Logic connectives
  - AND ( $\wedge$ ), OR ( $\vee$ ), NOT ( $\neg$ ), IMPLIES ( $\rightarrow$ )
  - light is on  $\rightarrow$  tank is full
  - (Light is off)  $\wedge$  (bulb is not broken)  $\rightarrow$  tank is empty
- Truth and falsity values – Truth Table 真值表

# 真值表 是逻辑规范/电路模型

## Truth Table is a Logic Specification/Model for Circuits

### NOT

<i>propositional variable</i>	<i>statement</i>
<u>P</u>	<u><math>\neg P</math></u>
<i>false</i>	<i>true</i>
<i>true</i>	<i>false</i>

<u>a</u>	<u><math>\bar{a}</math></u>
0	1
1	0

### AND

<u>P</u>	<u>Q</u>	<u><math>P \wedge Q</math></u>
<i>false</i>	<i>false</i>	<i>false</i>
<i>false</i>	<i>true</i>	<i>false</i>
<i>true</i>	<i>false</i>	<i>false</i>
<i>true</i>	<i>true</i>	<i>true</i>

<u>a</u>	<u>b</u>	<u><math>a \wedge b</math></u>
0	0	0
0	1	0
1	0	0
1	1	1

# Truth Table 真值表 (Contd.)

**OR**

$P$	$Q$	$P \vee Q$
<i>false</i>	<i>false</i>	<i>false</i>
<i>false</i>	<i>true</i>	<i>true</i>
<i>true</i>	<i>false</i>	<i>true</i>
<i>true</i>	<i>true</i>	<i>true</i>


a	b	$a \vee b$
0	0	0
0	1	1
1	0	1
1	1	1

# Building Blocks of Digital Circuits


## 数字线路的基本构件

### Building Blocks


### Truth Tables

 

AND gate  
 $c = a \wedge b$

 

OR gate  
 $c = a \vee b$

 


NOT  
 $c = \bar{a}$


a	b	$a \wedge b$
0	0	0
0	1	0
1	0	0
1	1	1

a	b	$a \vee b$
0	0	0
0	1	1
1	0	1
1	1	1


a	$\bar{a}$
0	1
1	0

 

NAND gate  
 $c = \overline{a \wedge b}$

 


NOR gate  
 $c = \overline{a \vee b}$

 


XOR gate  
 $c = \bar{a} \wedge b \vee a \wedge \bar{b}$

a	b	$\overline{a \wedge b}$	$\overline{a \vee b}$	$\bar{a} \wedge b \vee a \wedge \bar{b}$
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	0	0	0

 

2-1  
Multiplexor

If  $(e_0=0)$   $(f=a)$  else  $(f=b)$ ;

 


4-1  
Multiplexor


e1	e0	f
0	0	a
0	1	b
1	0	c
1	1	d



# Memory Design 存储器设计: bit and Byte

 


One-bit memory design

 

One bit can store a  
“1” or a “0”

 **8 bits = 1 Byte**  
**Can store**  
**a “character”**  
**Or a short *integer***



# Memory: Word, Long Word

存储器：字，长字

In a 32-bit computer:

4 Bytes = 1 word and 8 bytes = 1 double word

Word 字



Can store:  
*int* and *float*

double word 双字



Can store: a *long int* and a *double float*

# The Entire Memory, with 32-bit address space and byte-addressable


整个内存，32位地址空间和字节可寻址

Hex address	31	30	29	21	0
00000000h	1 byte	1 byte	1 byte	1 byte	
00000004h	1 byte	1 byte	1 byte	1 byte	
00000008h	1 byte	1 byte	1 byte	1 byte	
0000000Ch	1 byte	1 byte	1 byte	1 byte	
00000010h	1 byte	1 byte	1 byte	1 byte	
00000014h	1 byte	1 byte	1 byte	1 byte	
00000018h	1 byte	1 byte	1 byte	1 byte	
0000001Ch	1 byte	1 byte	1 byte	1 byte	
00000020h	1 byte	1 byte	1 byte	1 byte	
00000024h	1 byte	1 byte	1 byte	1 byte	
00000028h	1 byte	1 byte	1 byte	1 byte	
0000002Ch	1 byte	1 byte	1 byte	1 byte	
00000030h	1 byte	1 byte	1 byte	1 byte	
...	...	...	...	...	...
FFFFFFFF0h	1 byte	1 byte	1 byte	1 byte	
FFFFFFFF4h	1 byte	1 byte	1 byte	1 byte	
FFFFFFFF8h	1 byte	1 byte	1 byte	1 byte	
FFFFFFFFCh	1 byte	1 byte	1 byte	1 byte	

# Five Component Model of a Computer

## -- A Conceptual Model


### 计算机的5-部件概念模型

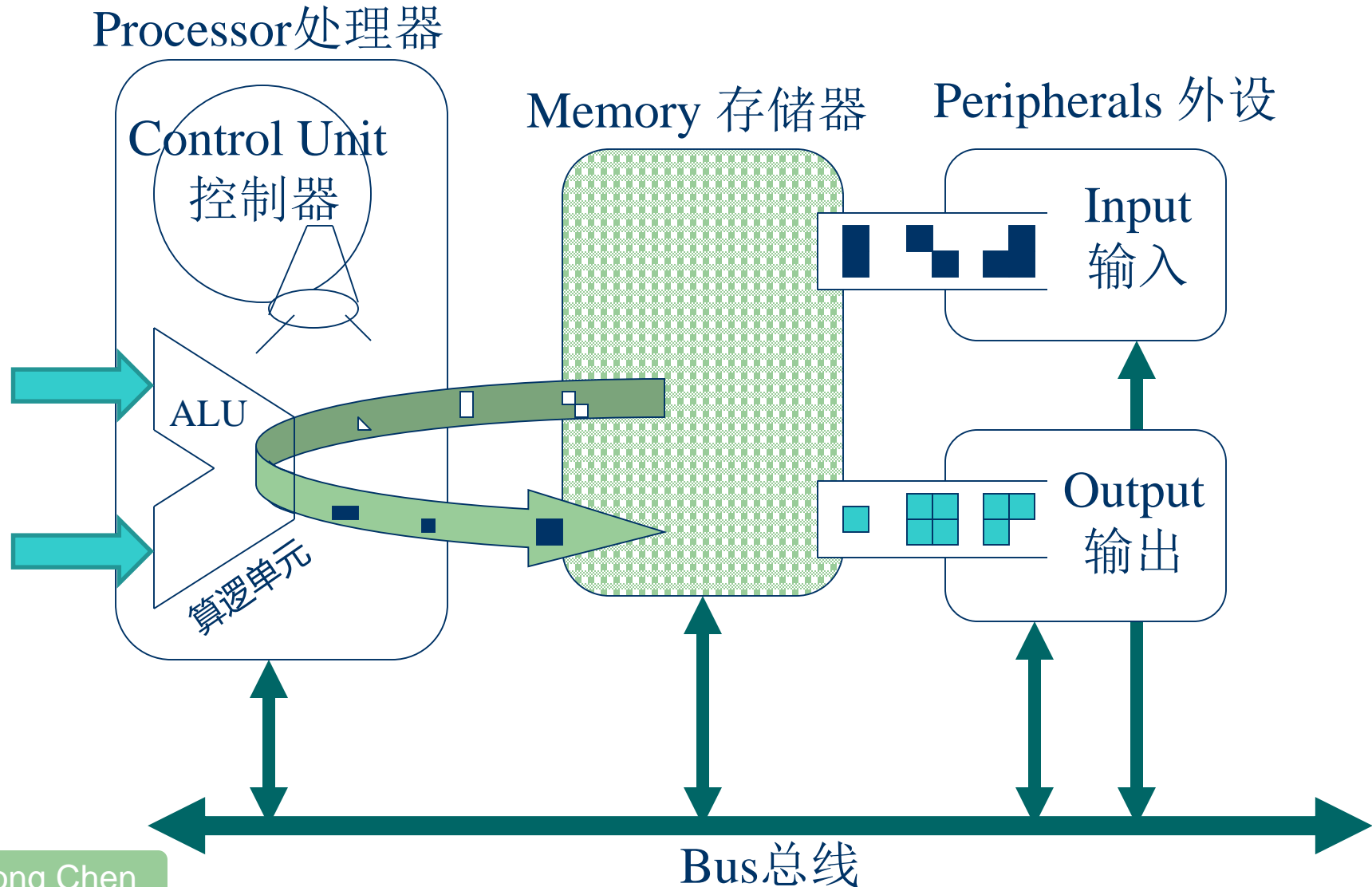

# Arithmetic/Logic Unit (ALU)

## 算术/逻辑单元

Operation code (3)

 

操作码 Operation code	功能 function
0 0 0	AND
0 0 1	OR
0 1 0	ADD
1 1 0	SUB




Adder

# Truth Table and Design of a One-Bit Adder

## 真值表和1-位加法器的设计

Truth Table


input			output	
a	b	carryIn	carryOut	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 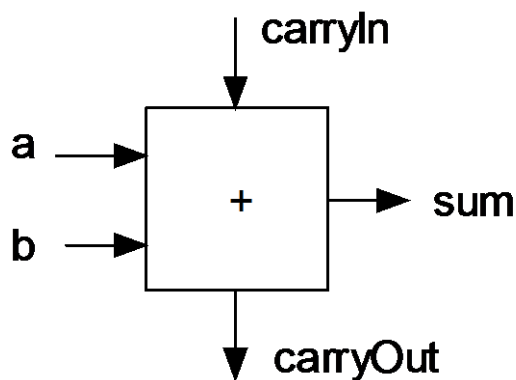 

One-bit adder

# One-Bit ALU Design 1位-ALU的设计


Inputs	carryOut	r
000001	d	0
000010	d	0

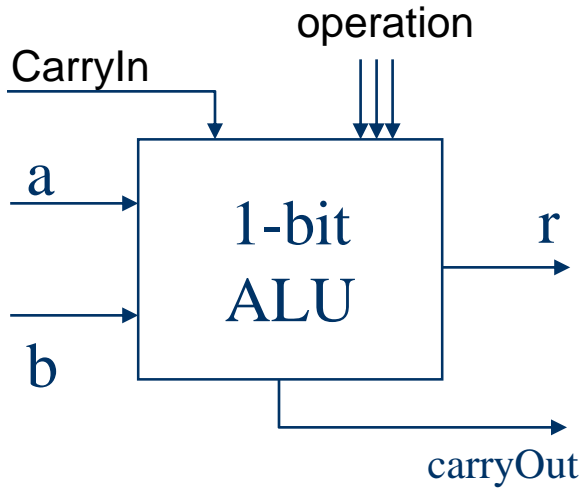

Six inputs and two outputs

Partial Truth Table



operation	function
0 0 0	AND
0 0 1	OR
0 1 0	ADD
1 1 0	SUB

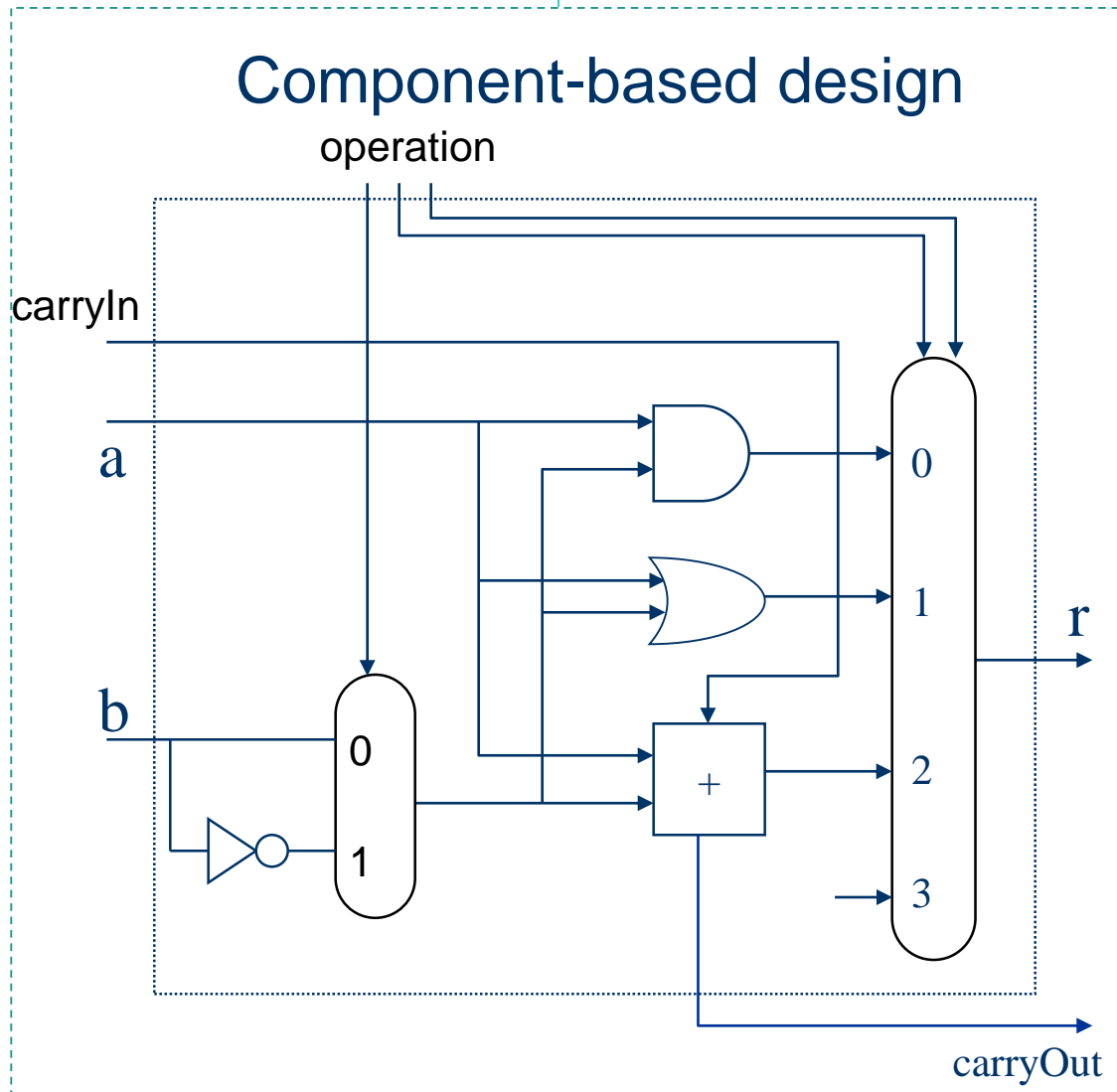

# 32-Bit ALU with 96 Inputs

32-ALU, 有96条输入线


operation	function
0 0 0	AND
0 0 1	OR
0 1 0	ADD
1 1 0	SUB

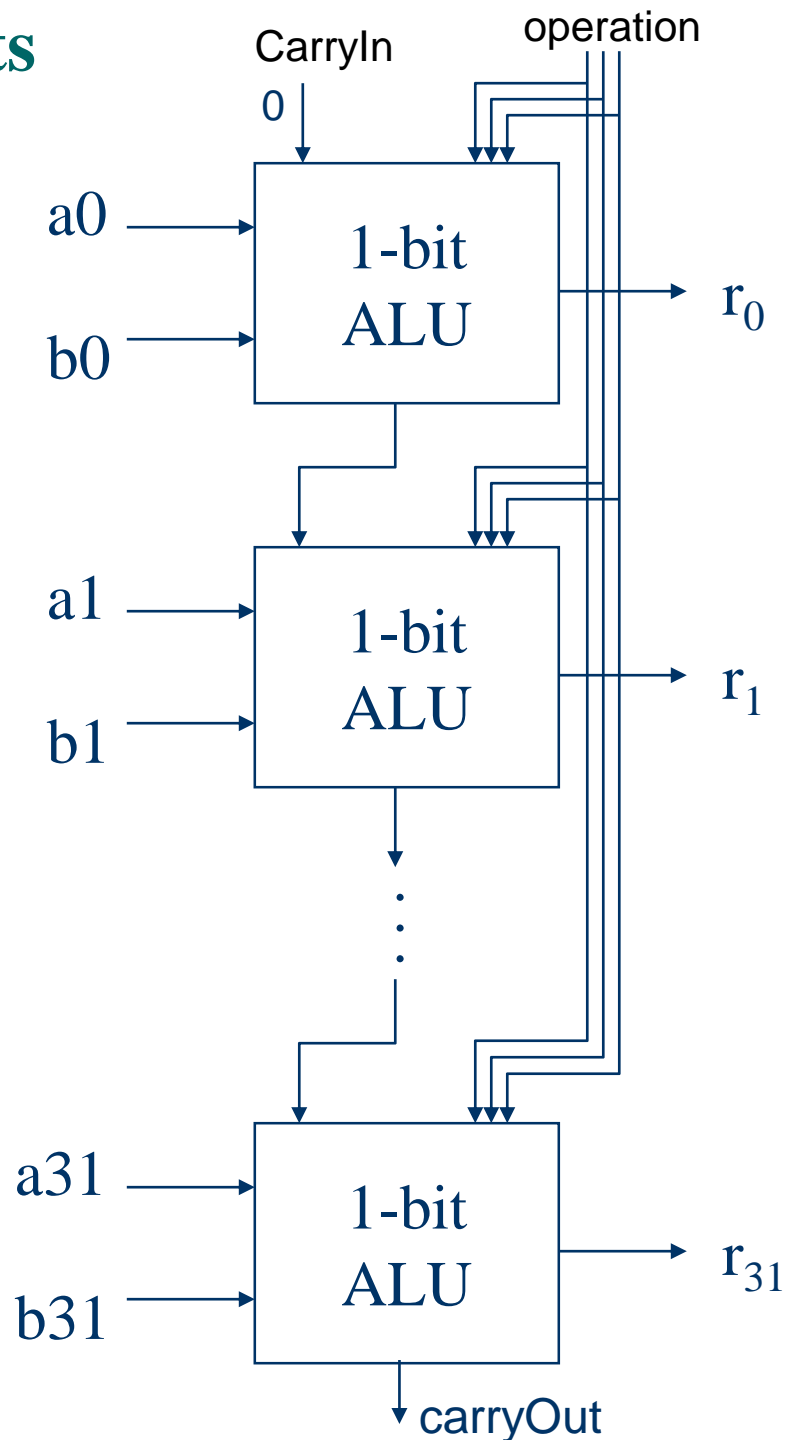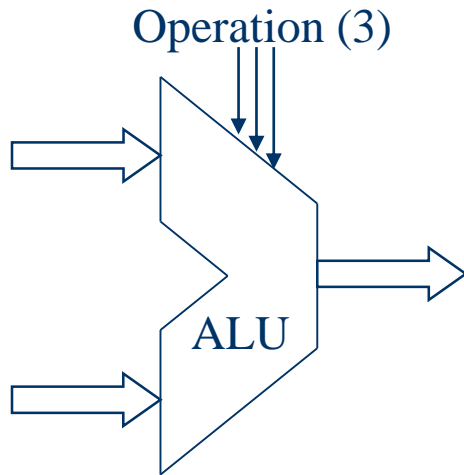




# Simulation of 1-bit Adder 1-位计算器仿真

One-bit adder logic design

 


VIPLE Implementation

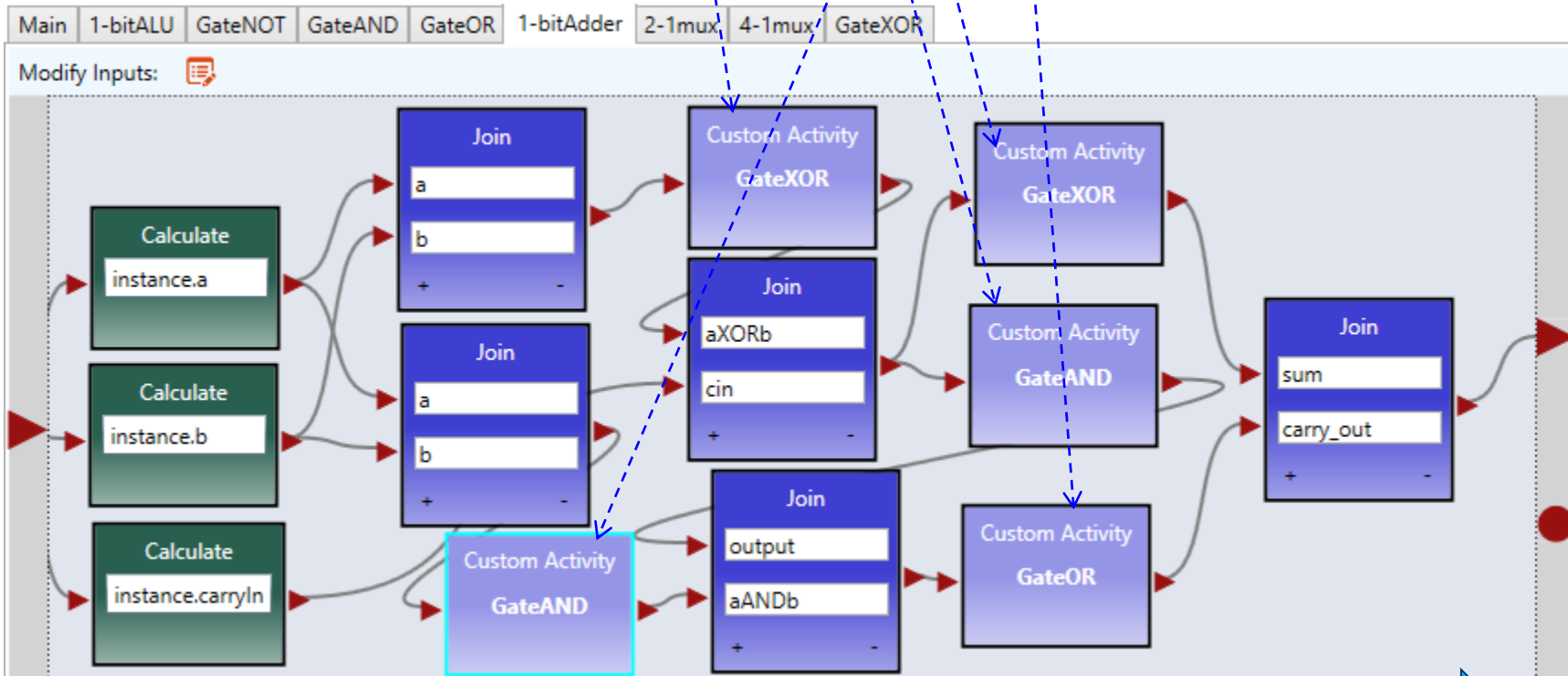

Define Before Using: Define the input whenever you see a warning sign

# Testing the One-Bit Adder 测试1-位加法器

Main Diagram

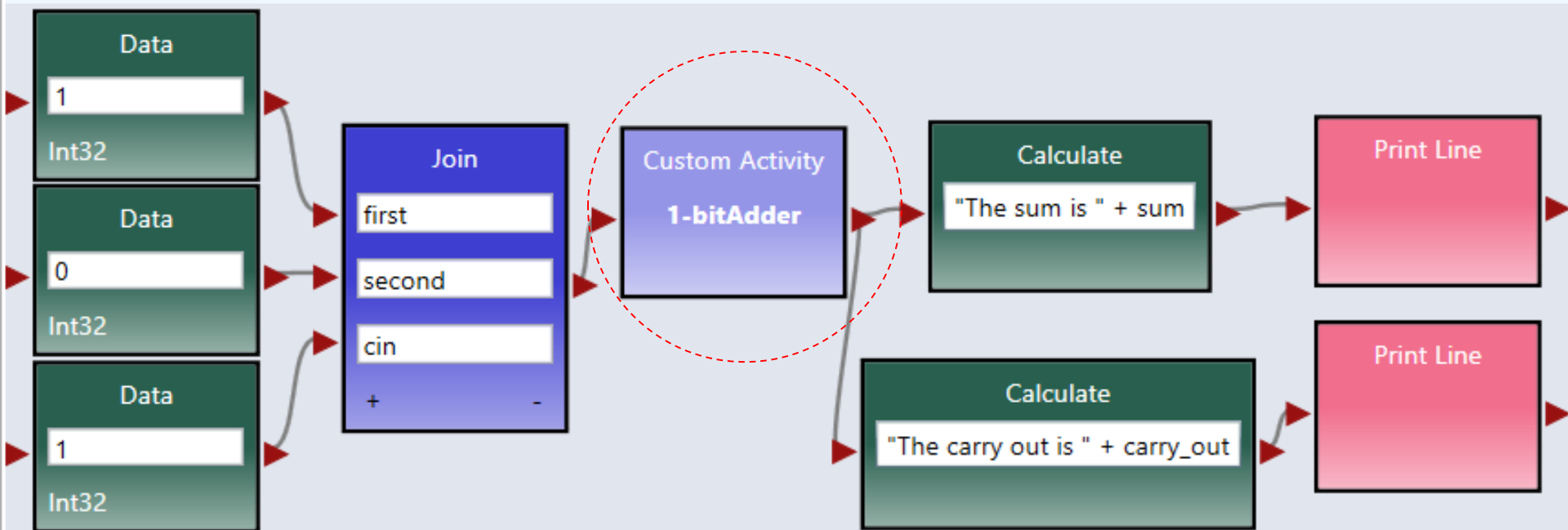

# Converting Decimal to Binary Pattern for Automated Test Case Generation

为自动测试输入生成，把二进制转换成十进制

CountTo7	a	b	carryIn
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1


if CountTo7 = 0, 1, 2, 3, then a = 0, else a = 1;

if CountTo7 = 0, 1, 4, 5, then b = 0, else b = 1;


if CountTo7 = 0, 2, 4, 6, then carryIn = 0, else carryIn = 1;

# Automated Test Case Generation

## 自动测试输入生成

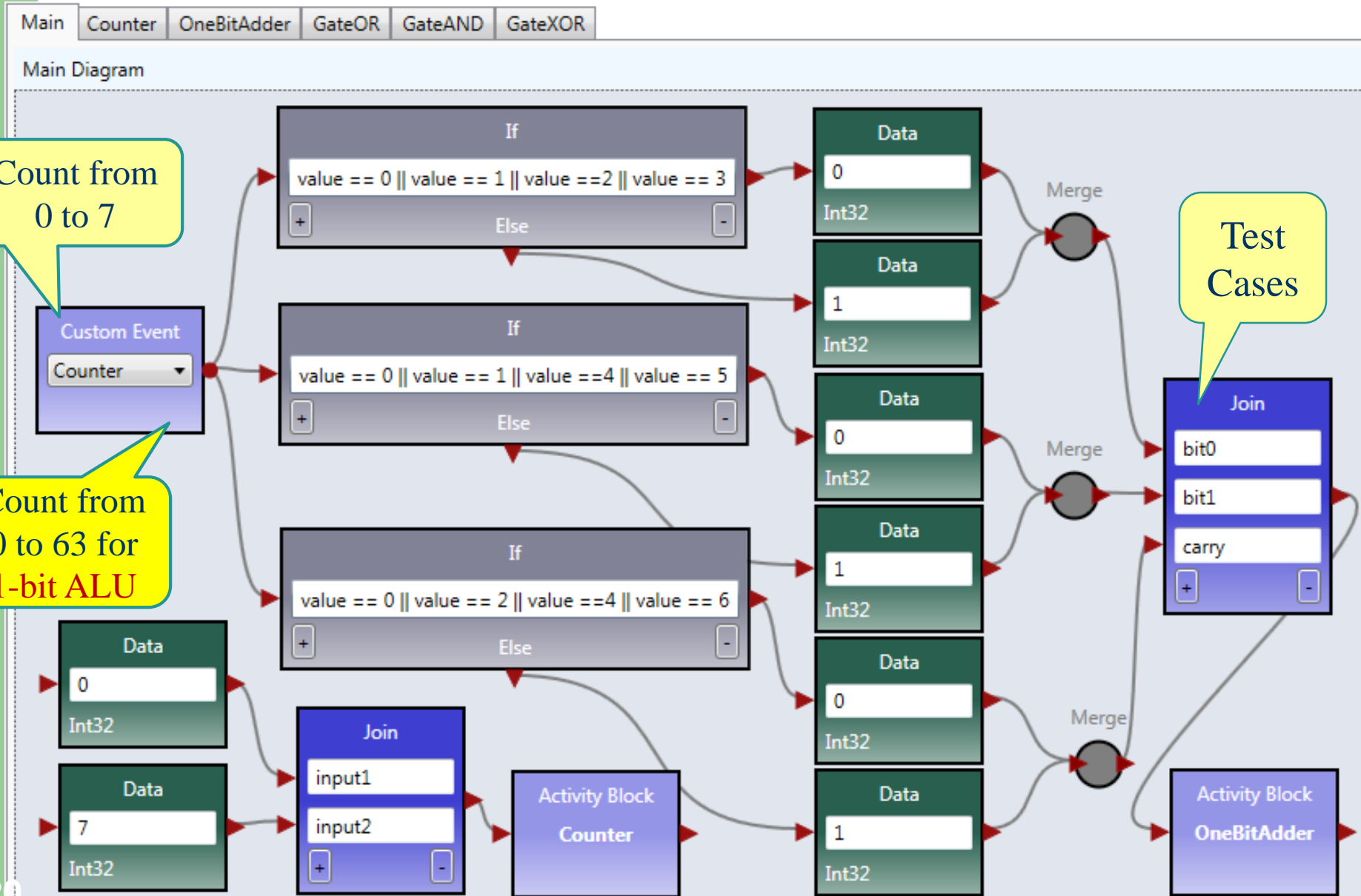


# One-Bit ALU 1-位算逻部件的设计

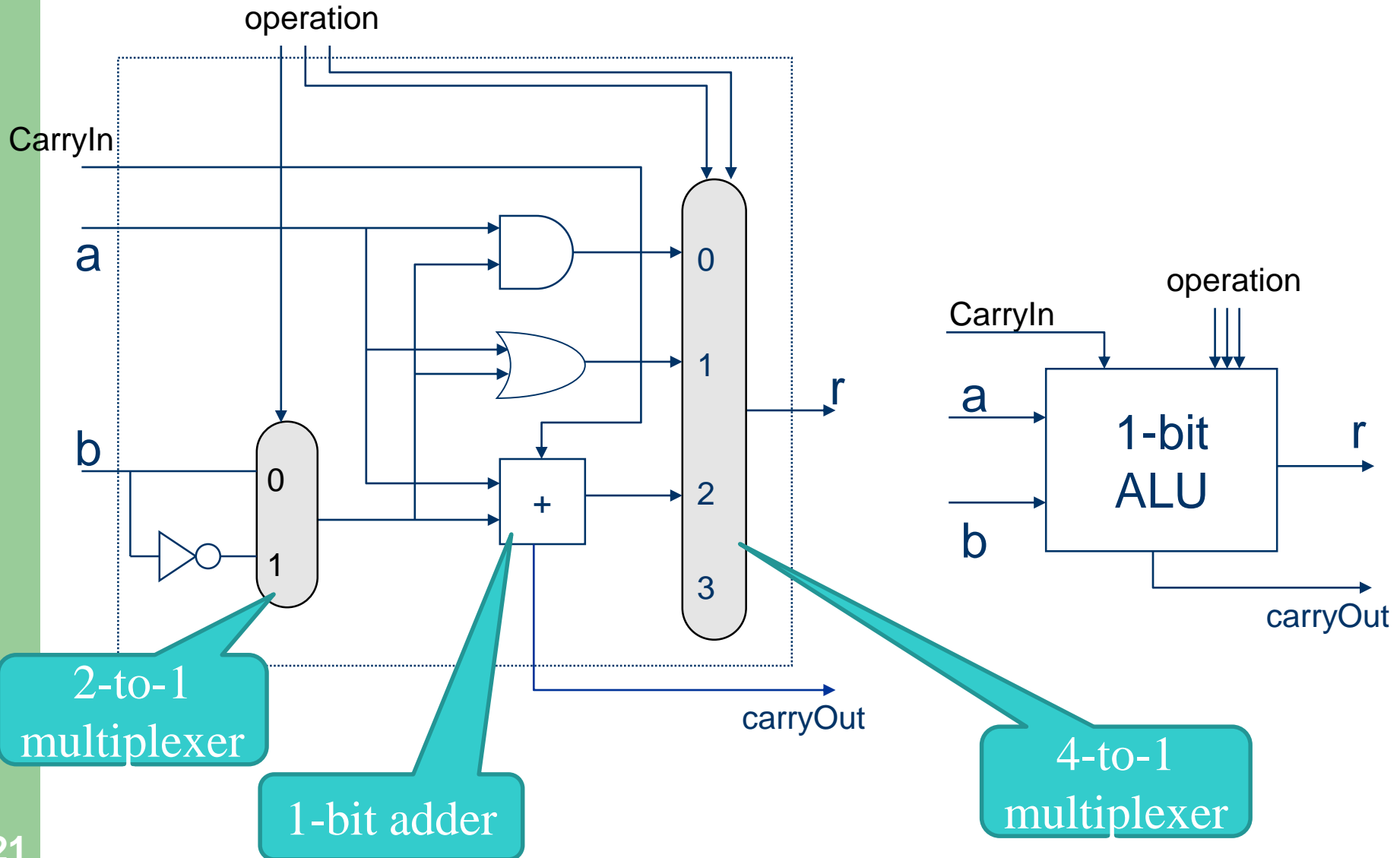


# One-Bit ALU VIPLE Implementation

## 1-位算逻部件的实现

Main 1-bitALU GateNOT GateAND GateOR 1-bitAdder 2-1mux 4-1mux GateXOR

Modify Inputs: 

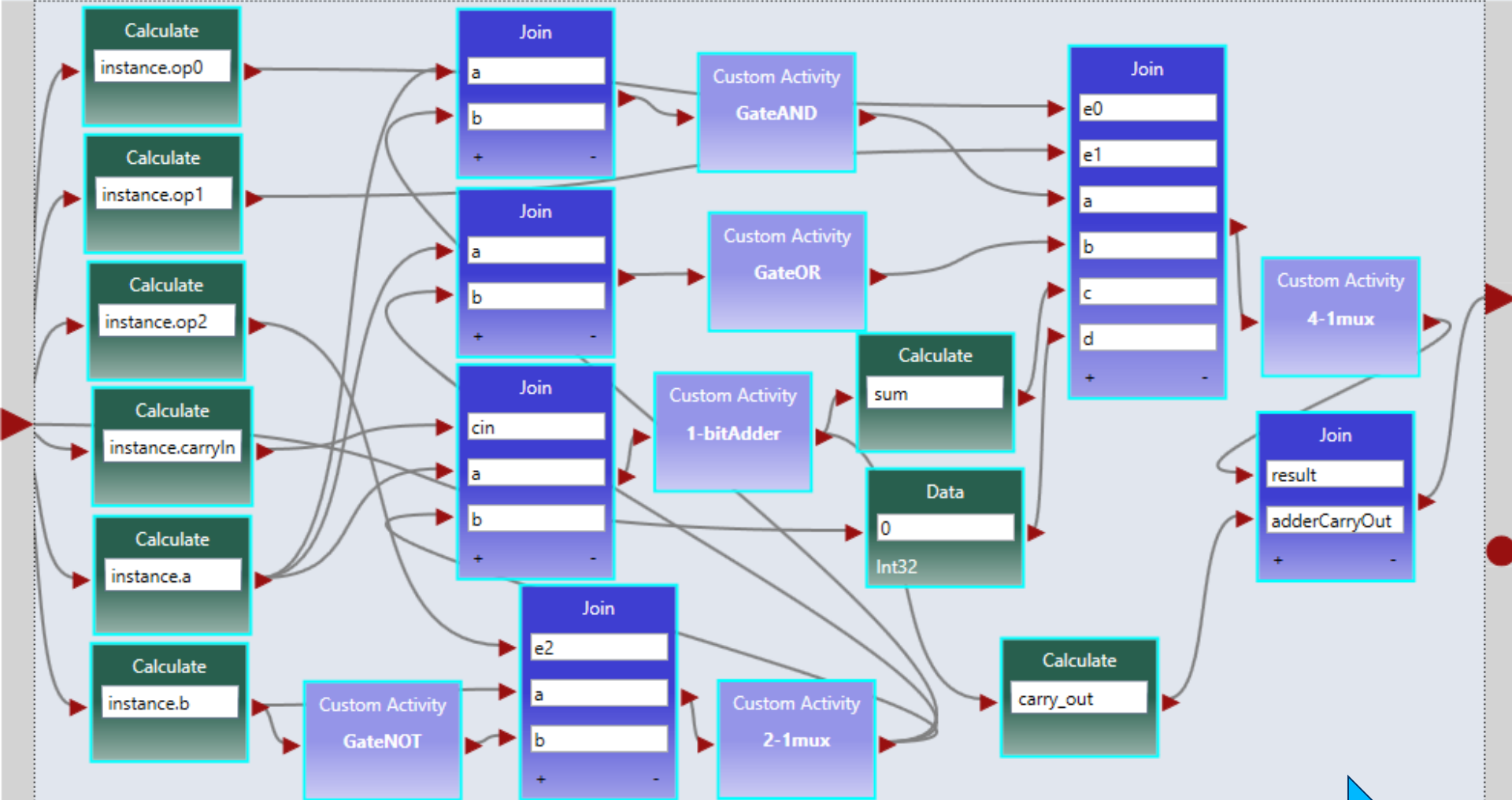


Yin

Define Before Using: Define the input whenever you see a warning sign

# Testing the One-Bit ALU 测试 1-位算逻辑部件的


Main Onebit\_ALU GateNOT 2-1Mux 4-1Mux OneBitAdder GateAND GateOR GateXOR

Main Diagram

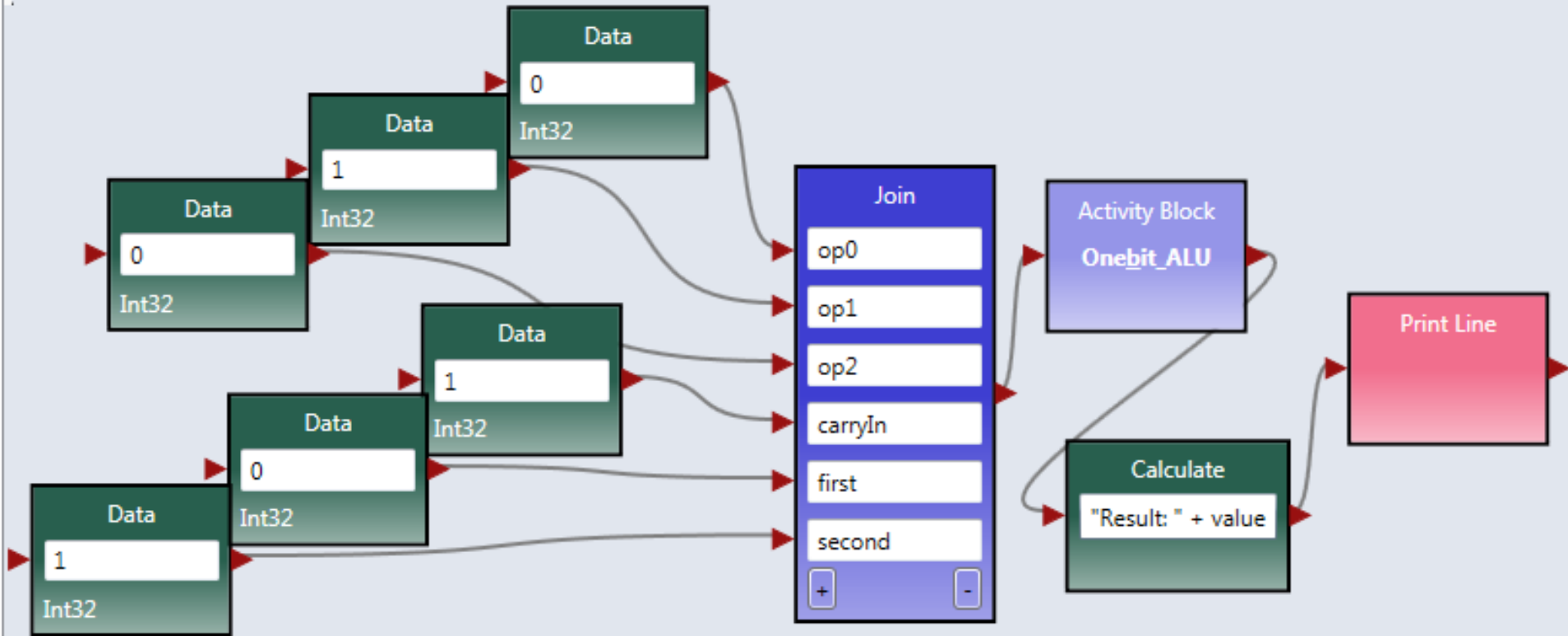

# Automated Test Case Generation

## 自动测试输入生成

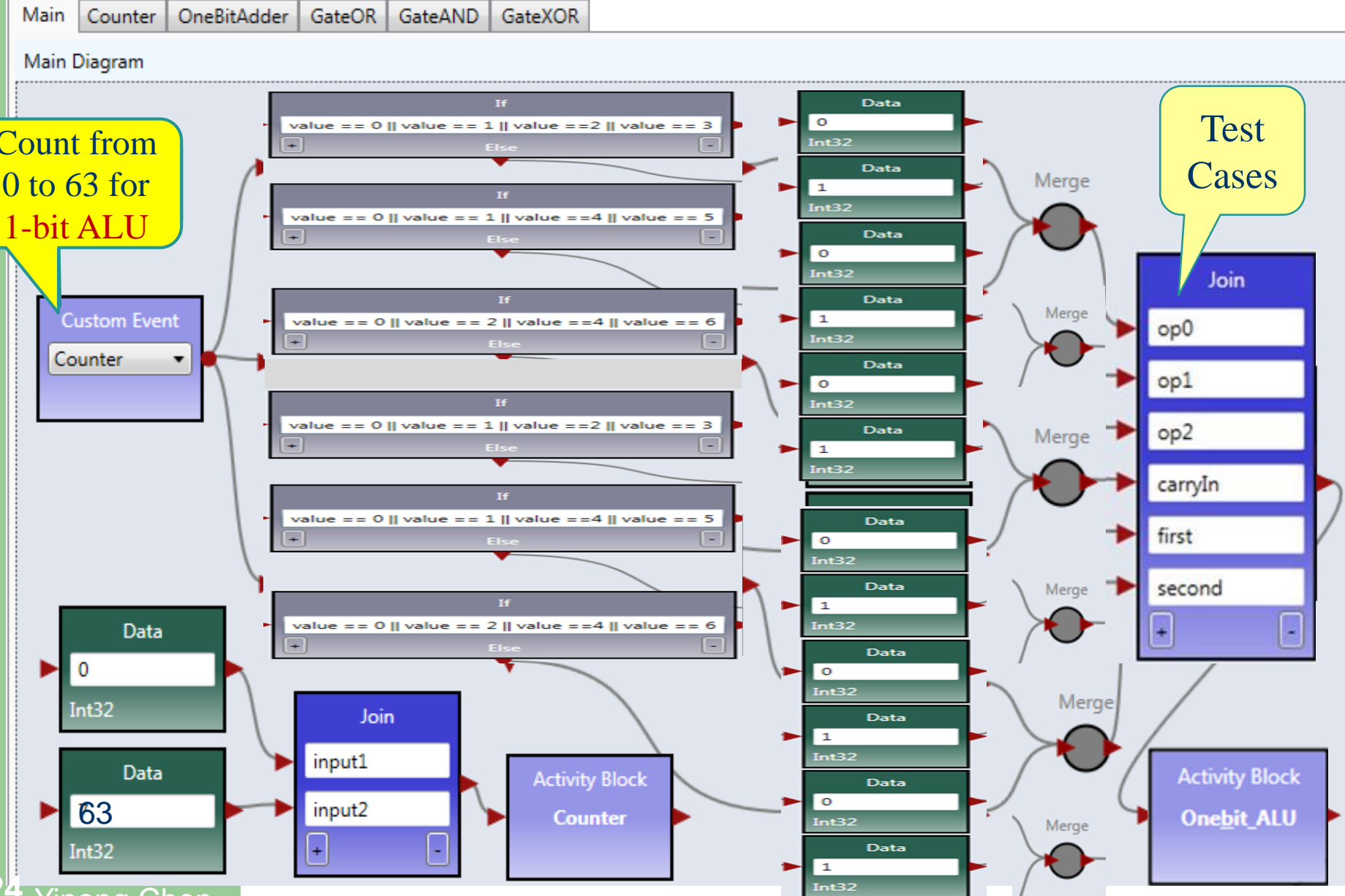

Count from 0 to 63 for 1-bit ALU

Test Cases