 



Lecture 4

Modeling, Analysis and Simulation in Logic Design



Dr. Yinong Chen

The Engineering Design Process

 

Contents



Logic Design and Specification in Truth Table



Building Blocks of Digital Systems



Memory Design




Arithmetic / Logic Unit (ALU) Design & Testing



Simulate a Design in VIPLE

Logic Design: Analogue versus Digital

tank

 


dial



empty


full

infinite range of values

 

tank

light : on / off
finite set of values

 

tank

Propositional Logic and its Elements

- Propositional logic is a language for modeling and specification
- Proposition: A statement that can either be true or false:
 - One plus two is three
 - There are two Nobel prize winners at Arizona State University
 - The sky is blue
 - How old are you?
 - You must ride a bike to school!
- Logic connectives
 - AND ($\wedge$), OR ($\vee$), NOT ($\neg$), IMPLIES ($\rightarrow$)
 - light is on $\rightarrow$ tank is full
 - (Light is off) $\wedge$ (bulb is not broken) $\rightarrow$ tank is empty
- Truth and falsity values – Truth Table

Truth Table is a Logic Specification/Model for Circuits

NOT

<i>propositional variable</i>	<i>statement</i>
<u>P</u>	<u>$\neg P$</u>
<i>false</i>	<i>true</i>
<i>true</i>	<i>false</i>

<u>a</u>	<u>$\bar{a}$</u>
0	1
1	0

AND

<u>P</u>	<u>Q</u>	<u>$P \wedge Q$</u>
<i>false</i>	<i>false</i>	<i>false</i>
<i>false</i>	<i>true</i>	<i>false</i>
<i>true</i>	<i>false</i>	<i>false</i>
<i>true</i>	<i>true</i>	<i>true</i>

<u>a</u>	<u>b</u>	<u>$a \wedge b$</u>
0	0	0
0	1	0
1	0	0
1	1	1

Truth Table (Contd.)


OR

P	Q	$P \vee Q$
<i>false</i>	<i>false</i>	<i>false</i>
<i>false</i>	<i>true</i>	<i>true</i>
<i>true</i>	<i>false</i>	<i>true</i>
<i>true</i>	<i>true</i>	<i>true</i>


a	b	$a \vee b$
0	0	0
0	1	1
1	0	1
1	1	1

Building Blocks of Digital Circuits


Building Blocks

 


AND gate
 $c = a \wedge b$

 


OR gate
 $c = a \vee b$

 


NOT
 $c = \bar{a}$

 

NAND gate
 $c = \overline{a \wedge b}$

 

NOR gate
 $c = \overline{a \vee b}$

 

XOR gate
 $c = \bar{a} \wedge b \vee a \wedge \bar{b}$


Truth Tables

a	b	$a \wedge b$
0	0	0
0	1	0
1	0	0
1	1	1

a	b	$a \vee b$
0	0	0
0	1	1
1	0	1
1	1	1


a	$\bar{a}$
0	1
1	0

a	b	$\overline{a \wedge b}$	$\overline{a \vee b}$	$\bar{a} \wedge b \vee a \wedge \bar{b}$
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	0	0	0

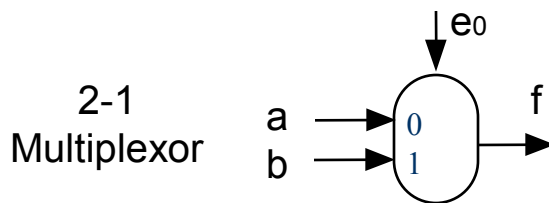


If ($e_0=0$) ($f=a$) else ($f=b$);

4-1
Multiplexor

 


e1	e0	f
0	0	a
0	1	b
1	0	c
1	1	d

Memory Design: bit and Byte

 


One-bit memory design

 

One bit can store a
“1” or a “0”

 8 bits = 1 Byte
Can store
a “character”
Or a short *integer*



Memory: Word, Long Word

In a 32-bit computer:

4 Bytes = 1 word and 8 bytes = 1 double word

word



Can store:
int and *float*

double word




Can store: a *long int* and a *double float*

The Entire Memory, with 32-bit address space and byte-addressable

Hex address	31	30	29	2	1	0
00000000h	1 byte	1 byte	1 byte	1 byte		
00000004h	1 byte	1 byte	1 byte	1 byte		
00000008h	1 byte	1 byte	1 byte	1 byte		
0000000Ch	1 byte	1 byte	1 byte	1 byte		
00000010h	1 byte	1 byte	1 byte	1 byte		
00000014h	1 byte	1 byte	1 byte	1 byte		
00000018h	1 byte	1 byte	1 byte	1 byte		
0000001Ch	1 byte	1 byte	1 byte	1 byte		
00000020h	1 byte	1 byte	1 byte	1 byte		
00000024h	1 byte	1 byte	1 byte	1 byte		
00000028h	1 byte	1 byte	1 byte	1 byte		
0000002Ch	1 byte	1 byte	1 byte	1 byte		
00000030h	1 byte	1 byte	1 byte	1 byte		
...	...	...	...	...		
FFFFFFFF0h	1 byte	1 byte	1 byte	1 byte		
FFFFFFFF4h	1 byte	1 byte	1 byte	1 byte		
FFFFFFFF8h	1 byte	1 byte	1 byte	1 byte		
FFFFFFFFCh	1 byte	1 byte	1 byte	1 byte		


Five Component Model of a Computer

-- A Conceptual Model

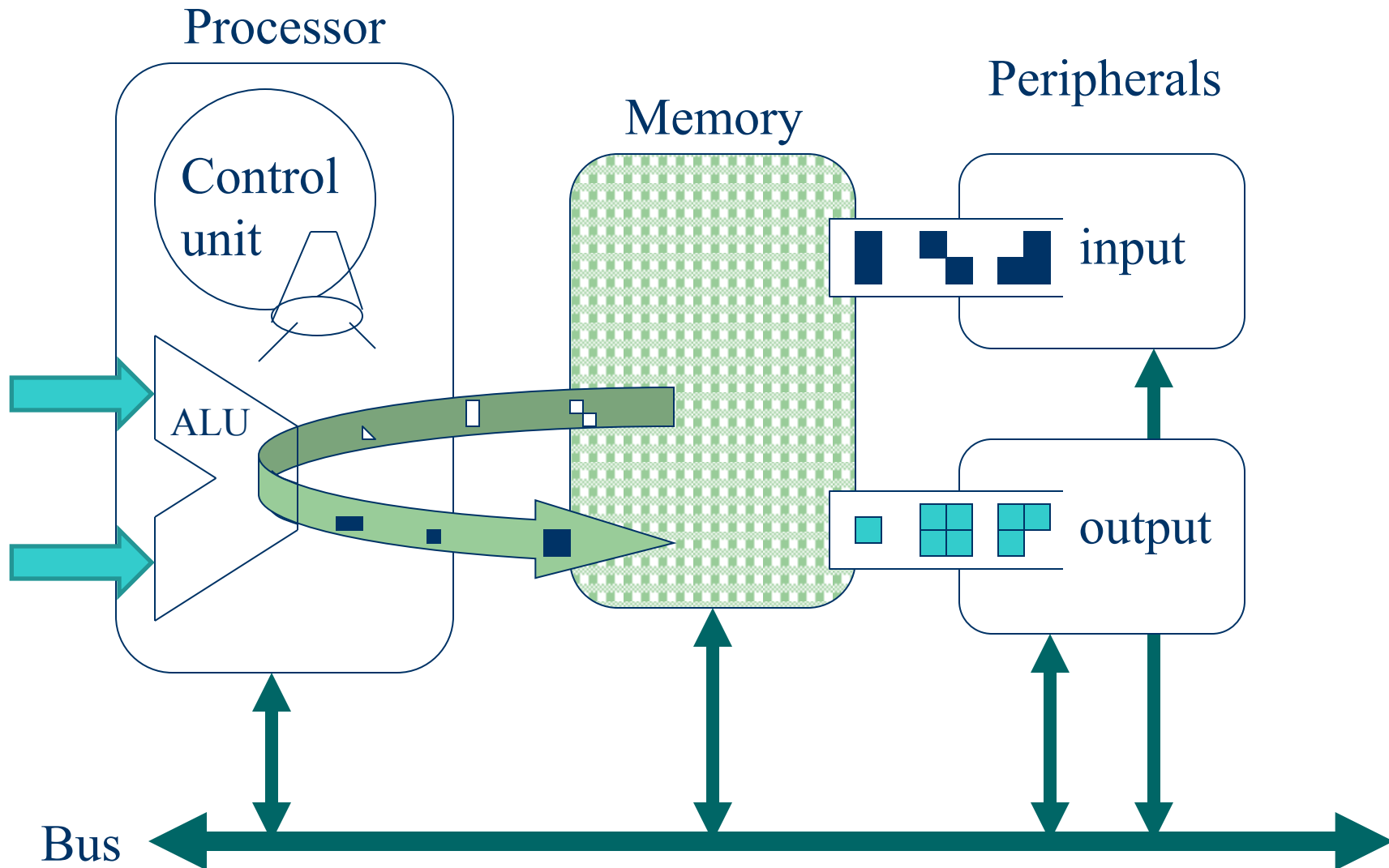

Arithmetic/Logic Unit (ALU)

Operation code (3)

 




Operation code	function
0 0 0	AND
0 0 1	OR
0 1 0	ADD
1 1 0	SUB

Adder

Truth Table and Design of a One-Bit Adder


Truth Table

input			output	
a	b	carryIn	carryOut	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

   

One-bit adder

ALU Design: One-Bit ALU

 


Six inputs and two outputs

Partial Truth Table

operation	function
0 0 0	AND
0 0 1	OR
0 1 0	ADD
1 1 0	SUB



Inputs	carryOut	r
000001	d	0
000010	d	0

Component-based design


 


32-Bit ALU with 96 Inputs

operation	function
0 0 0	AND
0 0 1	OR
0 1 0	ADD
1 1 0	SUB

  


Simulation of 1-bit Adder

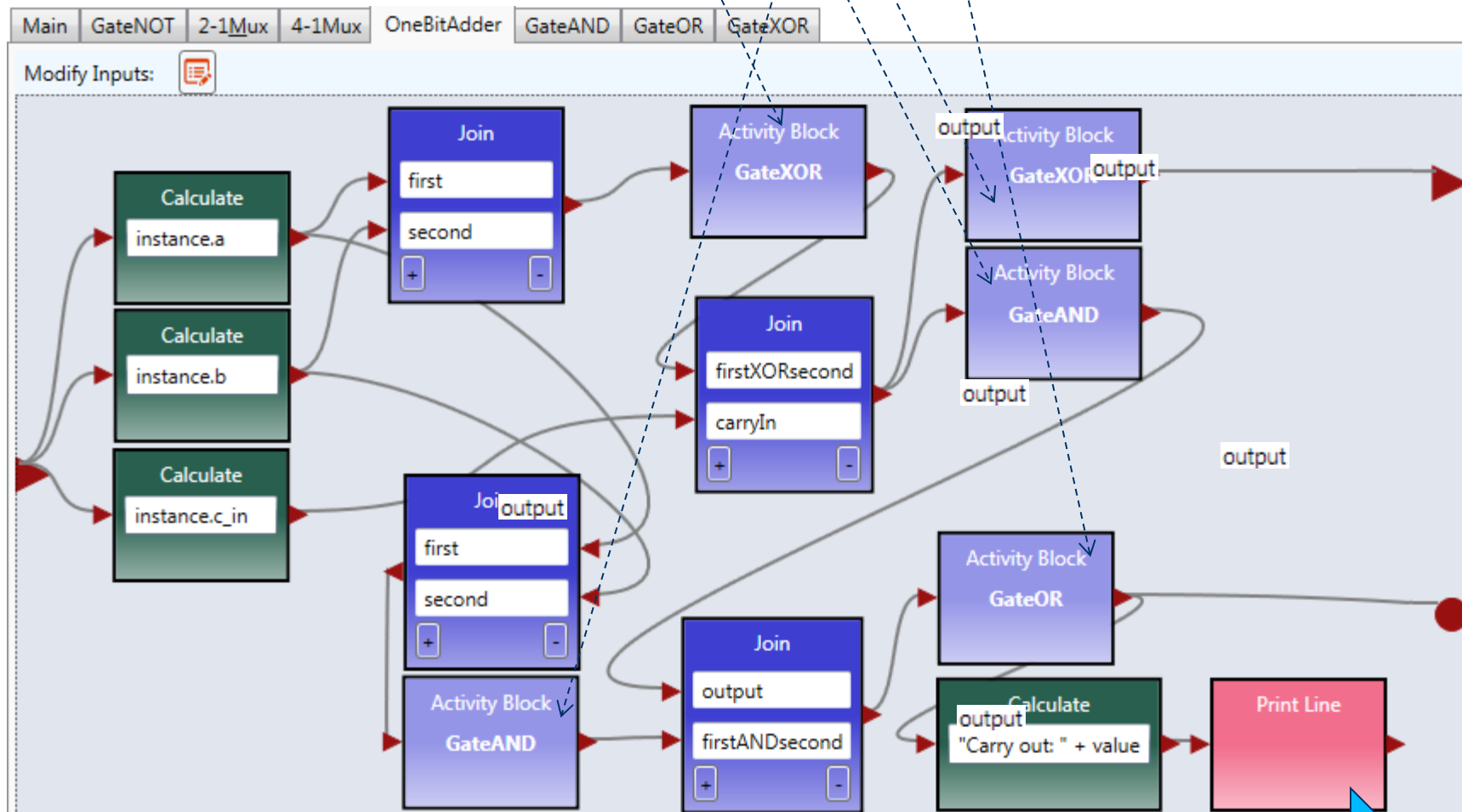 


Define Before Using: Define the input whenever you see a warning sign

Testing the One-Bit Adder

 

Convert Activity to Service

Right click

 

Converting Decimal to Binary Pattern for Automated Test Case Generation


CountTo7	a	b	carryIn
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1

if CountTo7 = 0, 1, 2, 3, then a = 0, else a = 1;


if CountTo7 = 0, 1, 4, 5, then b = 0, else b = 1;

if CountTo7 = 0, 2, 4, 6, then carryIn = 0, else carryIn = 1;


Automated Test Case Generation

 

One-Bit ALU

 

One-Bit ALU VIPLE Implementation

 


Define Before Using: Define the input whenever you see a warning sign

Testing the One-Bit ALU

Main Onebit_ALU GateNOT 2-1Mux 4-1Mux OneBitAdder GateAND GateOR GateXOR

Main Diagram

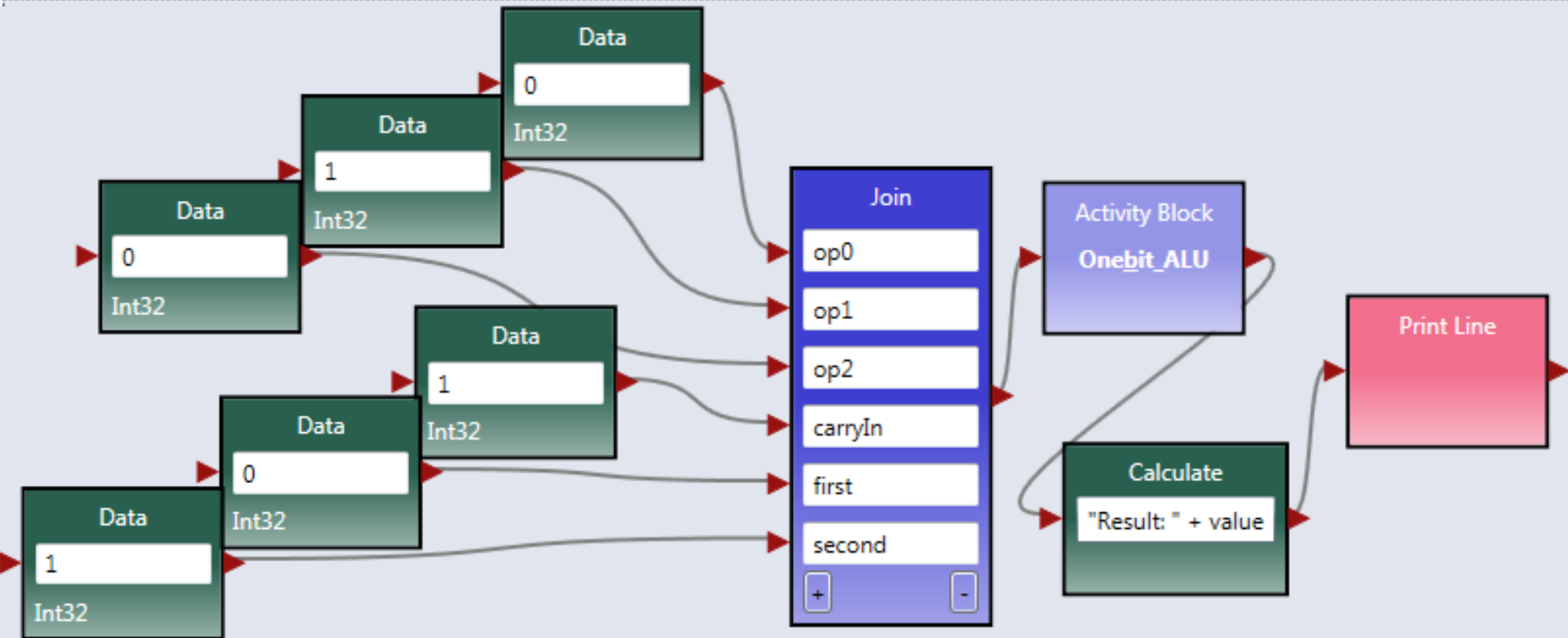

Automated Test Case Generation

